

Q1: NOV 2001 P2

- 4 A network of resistors, each of resistance $6.0\ \Omega$, is constructed as shown in Fig. 4.1.

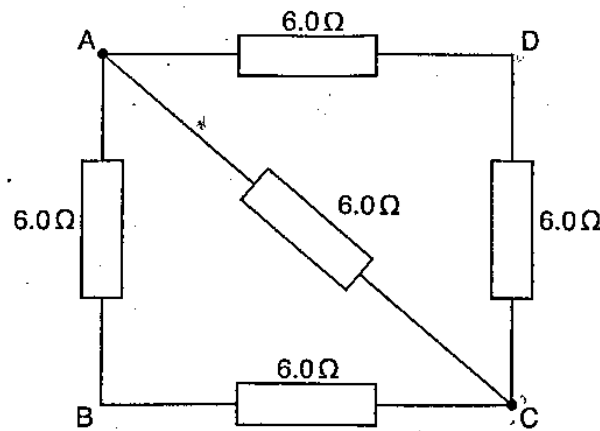


Fig. 4.1

Determine the total resistance of the network between

- (a) terminals A and C,

resistance = Ω [2]

- (b) terminals A and D.

resistance = Ω [3]

Q2: NOV 2004 P2

- 4 (a) State Kirchhoff's laws.

[2]

- (b) Fig. 4.1 shows a circuit with resistors R_1 and R_2 of resistance $2\ \Omega$ and $3\ \Omega$ respectively. The circuit includes three cells of e.m.f. $E_1 = 12\text{ V}$, $E_2 = 10\text{ V}$ and $E_3 = 8\text{ V}$. Each of the cells has an internal resistance of $1\ \Omega$.

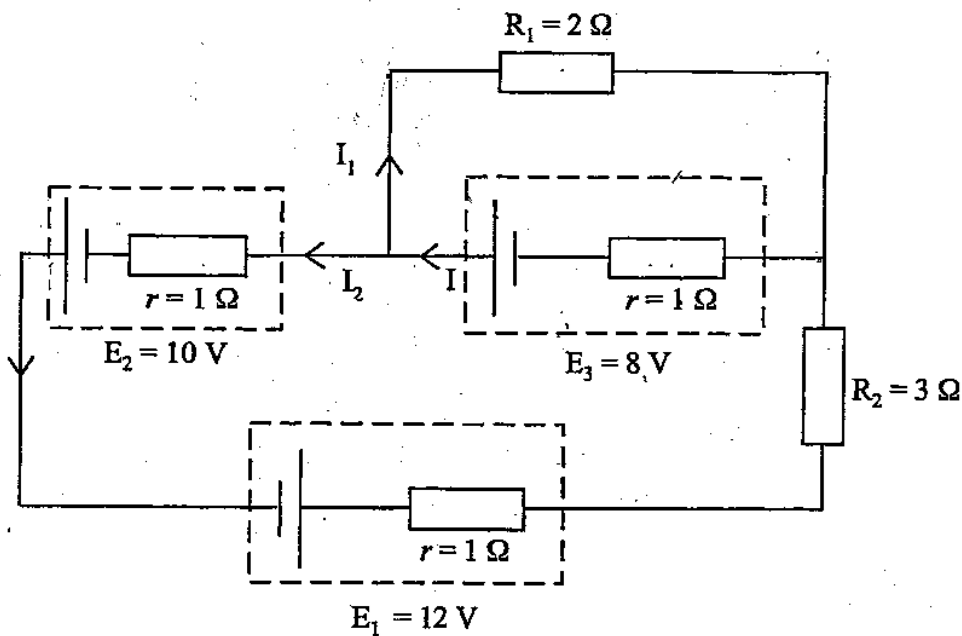


Fig. 4.1

- (i) Use arrows to identify two loops in Fig. 4.1.

[2]

- (ii) Given that $I_1 = 1.06\text{ A}$, calculate I_2 .

$I_2 =$ _____

[4]

Q3: NOV 2009 P2

- 5 (a) A potentiometer is used to measure *e.m.f.* and *p.d.* to a high accuracy.

Distinguish between *e.m.f.* and *p.d.* in terms of energy considerations.

[2]

- (b) Fig. 5.1 shows a potentiometer circuit for measuring the *e.m.f.* of a test cell X.

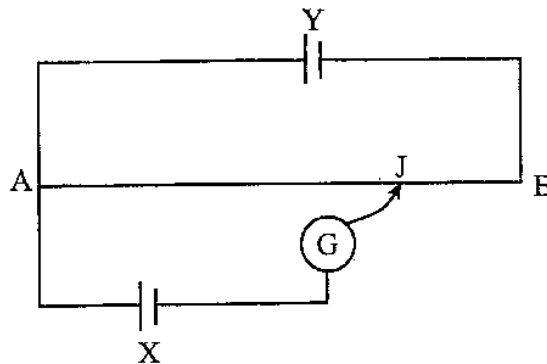


Fig. 5.1

- (i) Identify cell Y and its function.

[2]

- (ii) The slider J should not be moved continuously along the wire.
Explain why.

[1]

Q4:JUN 2011 P2

6 (i) State Kirchoff's two laws.

1. _____

2. _____

(ii) State the respective quantity conserved in each law.

1. _____
2. _____

[4]

Q5:JUN 2014 P2

6 (a) State and explain Kirchhoff's first and second laws.

first law:


explanation: _____

second law:

explanation: _____

[4]

(b) Fig. 6.1 shows a simple circuit.

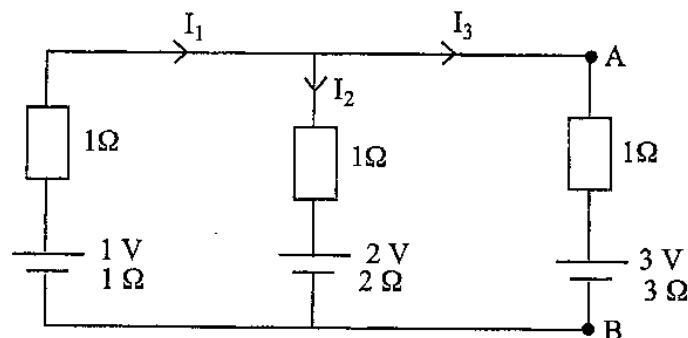

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : R. Nuzo

- (i) Calculate the values of I_1 , I_2 and I_3 .

$$I_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}}$$

[6]

- (ii) Hence determine the potential difference between points A and B.


$$p.d. = \underline{\hspace{2cm}} \quad [1]$$

Q6:JUN 2017 P2

- (a) A cell has an e.m.f. of 3V.
Explain the underlined phrase.

[1]

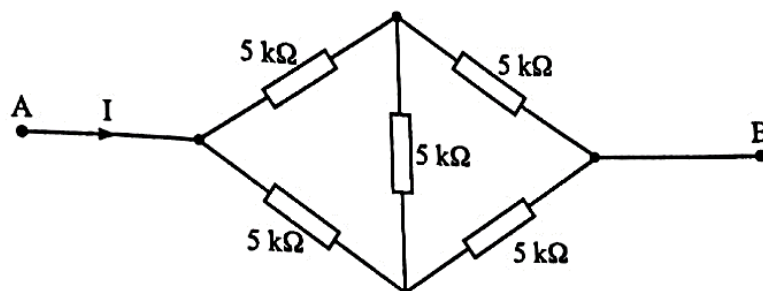- (b) Fig. 4.1 shows a connection of resistors of $5\text{ k}\Omega$ each.



4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : R. Nuzar

The *p.d* across A and B is 3 V.

Determine the

- (i) total resistance between A and B,

resistance = _____

- (ii) current, *I*, in the circuit.

current = _____

[5]

Q7:NOV 2018 P2

- 5 The LDR in Fig. 5.1 has a resistance of $1\text{ K}\Omega$ in light and $1\text{ M}\Omega$ in darkness. The battery has negligible internal resistance.

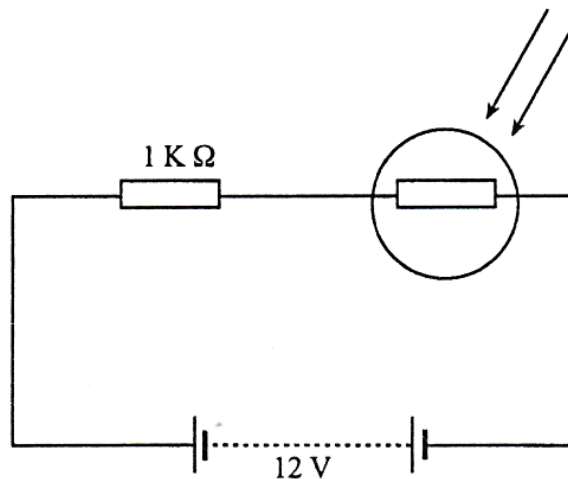


Fig. 5.1

- (a) Calculate the voltage across the LDR when in darkness.

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : *R. Nuga*

- (b) A student connects a 12 V lamp of resistance $10\ \Omega$ across the LDR so that the lamp will automatically light in darkness and turn off in bright light.

State and explain whether the student will be successful or not.

Q8:2018 SPEC P2

5. When a slide wire potentiometer is used to measure the *emf* of a cell, a balance point cannot be found along the resistance wire.

Explain how a voltmeter may be used to discover the cause of the problem.

[3]

Q9:NOV 2002 P3

- 4 (f) A light-dependent resistor (LDR) is connected in series with a $10\text{ k}\Omega$ resistor and a 12 V d.c. supply as shown in Fig. 4.1.

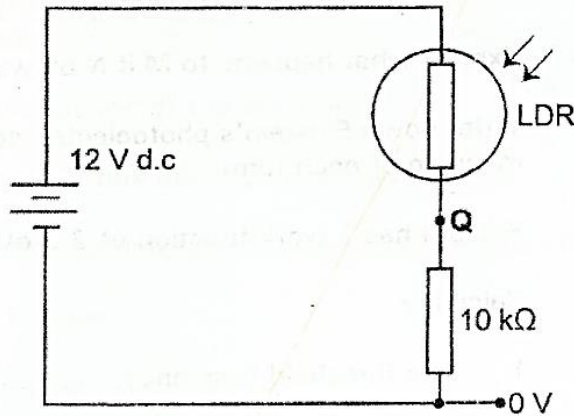


Fig. 4.1.

Find the potential at the point **Q** when the LDR is

- (i) in the dark and has a resistance of $60\text{ k}\Omega$.
 - (ii) in bright sunlight and has a resistance of $2\text{ k}\Omega$.
- (g) What is the resistance of the LDR if the potential at **Q** is 3.5 V .
- (h) Two lamps **M** and **N** labelled $3\text{ V}, 0.20\text{ A}$ and $6\text{ V}, 0.06\text{ A}$ respectively, light up with normal brightness (see Fig 4.2).

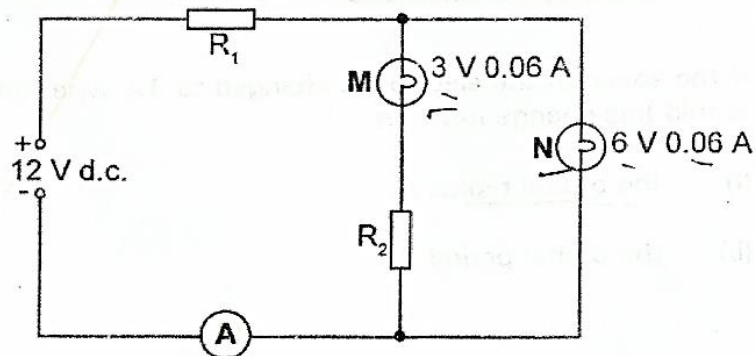


Fig. 4.2

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : R. Nuzo

- (i) Determine the values of R_1 and R_2 .
- (ii) What is the ammeter reading?
- (iii) Explain what happens to M if N blows out.

[4]

Q10:NOV 2007 P3

- 4 (a) Define *potential difference* and the *volt*. [2]
- (b) A voltmeter was connected to measure the potential difference across the $10.0 \text{ k}\Omega$ resistor as in Fig. 4.1. The potential difference was found to be 3.1 V .

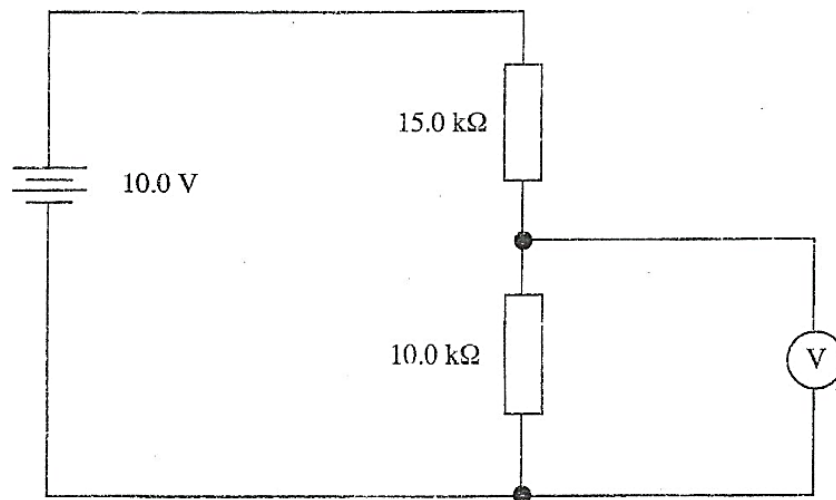


Fig. 4.1

- (i) Calculate the potential difference across the $10.0 \text{ k}\Omega$ resistor before the voltmeter is connected.
- (ii) Compare and comment on the two values of the potential difference.
- (iii) Calculate the resistance of the voltmeter. [7]

Q11:JUN 2019 P3

- 3 (a) (i) Define *potential difference*.
- (ii) State and explain the effect of internal resistance of a power source on its terminal potential difference.
- (iii) Fig. 3.1 shows a current of 1.5 A being driven through a circuit by a battery of emf 9.0 V and internal resistance 2.0Ω .

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : R. Nuzo

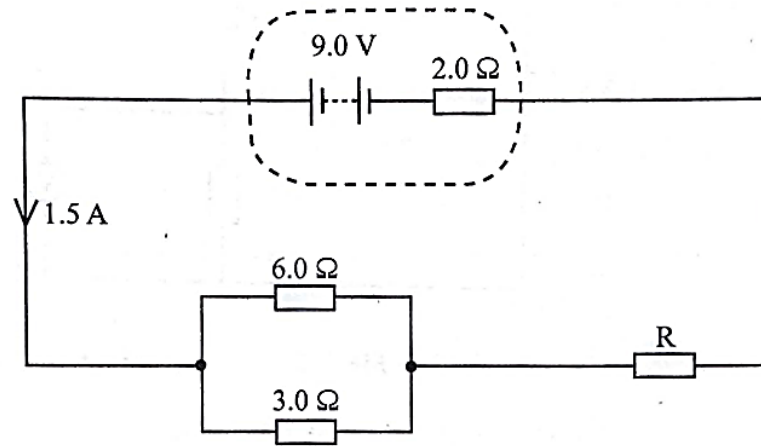


Fig. 3.1

Determine the

1. current flowing through the 6.0 Ω resistor,
2. amount of charge that passes through the 6.0 Ω resistor in 5.0 minutes,
3. value of the resistor, R.

[8]

- (b) Fig. 3.2 shows a potential divider circuit with a cell of emf 1.5 V and negligible internal resistance. The voltmeter has an infinite resistance. At 0 °C the thermistor has a resistance of 3.9 kΩ and the voltmeter reads 1.0 V.

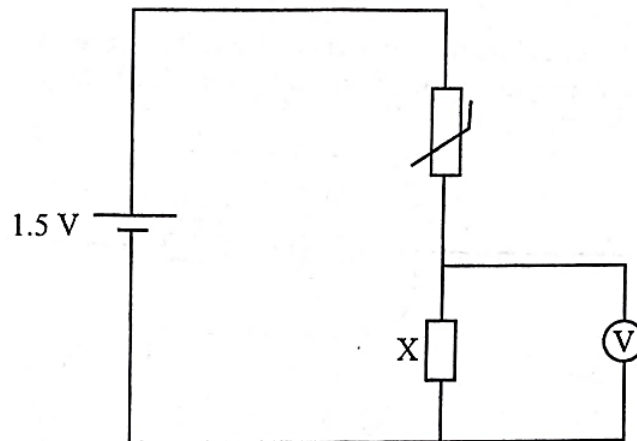


Fig. 3.2

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : R. Nuga

- (i) Determine the
 1. resistance of the fixed resistor X,
 2. voltmeter reading at 30°C when the thermistor has a resistance of $1.3\text{ k}\Omega$.
- (ii) Suggest a practical use of this circuit.

[5]

Q12:NOV 2009 P5

2

- (a) State Kirchhoff's laws.

[2]

- (b) Fig. 2.1 shows a circuit for the supply of energy to a load of $6.0\text{ }\Omega$.

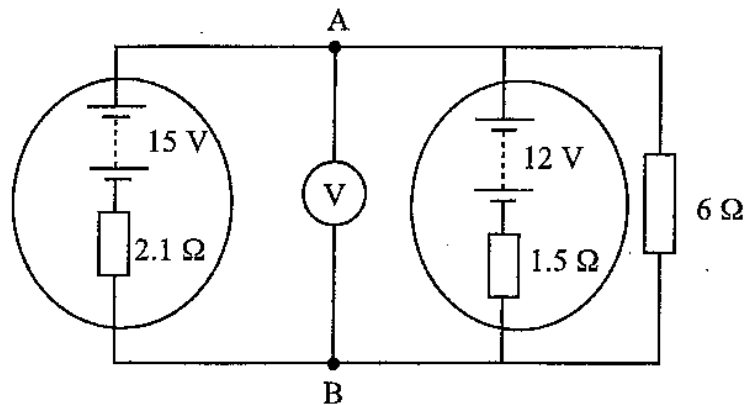


Fig. 2.1

A high resistance voltmeter is connected to the points A and B.

- (i) Calculate the currents through the power supplies and the load.
- (ii) Deduce the voltage recorded by the voltmeter.
- (iii) Calculate the power dissipated in the load.

[10]

Q13:JUN 2009 P5

- 2 (a) State Kirchhoff's laws and give the principle from which each is derived. [4]
- (b) Fig. 2.1 shows a circuit in which the voltmeter is used to measure p.d.

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : R. Nuzo

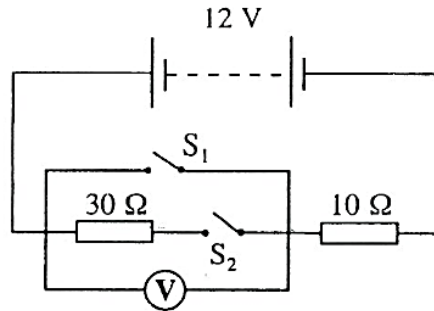


Fig. 2.1

State, giving reasons, the voltmeter reading when

- (i) only S_1 is closed,
- (ii) only S_2 is closed,
- (iii) both S_1 and S_2 are open,
- (iv) both S_1 and S_2 are closed.

[4]

Q14:NOV 2011 P5

- 3 (a) Draw a circuit symbol for a galvanometer. [1]
- (b) Using a standard cell with e.m.f. of 1.0186 V, explain how you would find the e.m.f. E_1 of a torch cell using a potentiometer. [3]

- (c) Fig. 3.1 shows current flowing through a junction. Fig. 3.2 shows a closed loop.

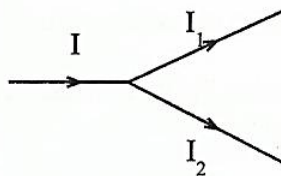


Fig. 3.1

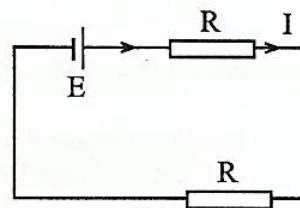


Fig. 3.2

- (i) Explain why
 - 1. $I = I_1 + I_2$,
 - 2. $E = \Sigma IR$.

4.2 D.C CIRCUITS P2, P3&P5 QUESTIONS

Compiled by : *R. Nuzo*

- (ii) Use the concepts in (i) to find current I_1 and I_2 in Fig. 3.3.

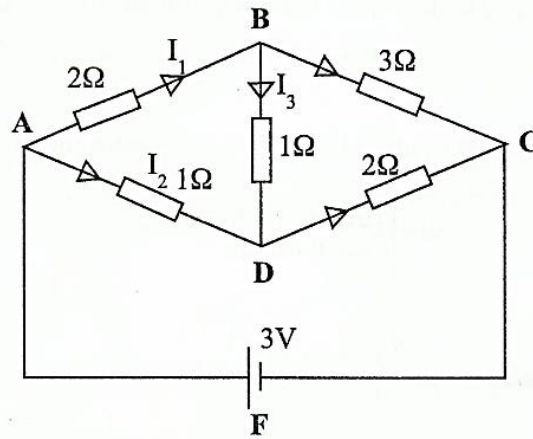


Fig. 3.3

[8]

Q15:JUN 2013 P5

- 1 (b) Fig. 1.1 shows a circuit with a power supply of e.m.f, E , and negligible internal resistance.

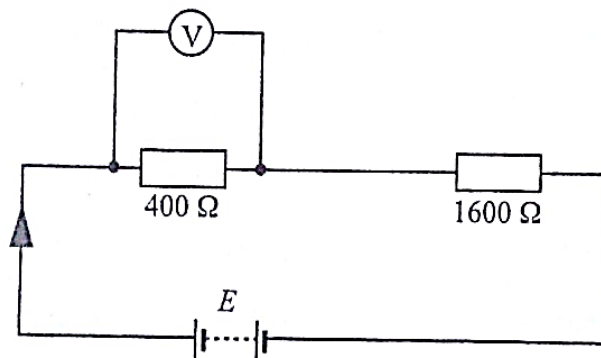


Fig. 1.1

- (i) If the resistance of the voltmeter is $2\,000\,\Omega$, calculate the magnitude of E when the voltmeter gives a reading of 8 V .
- (ii) Suggest **one** assumption made besides that of negligible internal resistance.

[4]

Q16:JUN 2014 P5

- 2 (a) (i) State Kirchhoff's laws and in each case indicate the significance of the law.
- (ii) Show that the combined resistance, R_T , of three resistors connected in series is given by $R_T = R_1 + R_2 + R_3$.
- (iii) A battery charger is connected to a rechargeable cell as shown in Fig. 2.1.

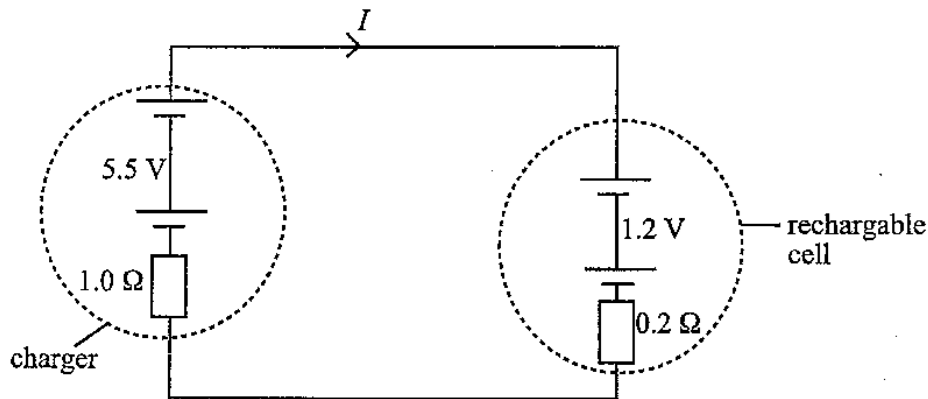


Fig. 2.1

Calculate the current through the rechargeable cell.

[8]

- (b) Sketch and explain the I - V characteristic for a semi-conductor diode.

[4]

Q17:NOV 2014 P5

- 2 (a) (i) Define *resistance* and *ohm*.
- (ii) Calculate the electrical resistance of a wire of length 0.75 km, cross-sectional area 60 cm^2 and resistivity $1.0 \times 10^{-7} \Omega\text{m}$.

[4]

- (b) A light dependent resistor in the potential divider circuit shown in Fig. 2.1, has a resistance which varies between $1\,000 \Omega$ in bright light and $5.00 \text{ M}\Omega$ in darkness.

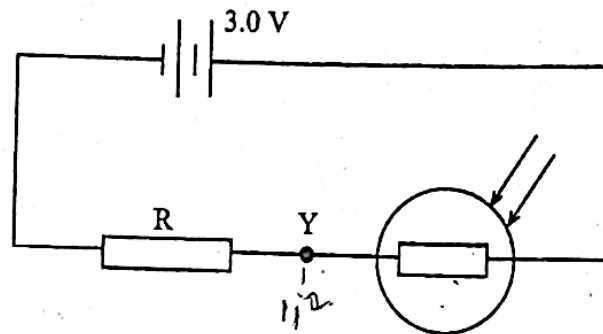


Fig. 2.1

Calculate the value of the series resistor, R , which is needed so that the potential at Y is 1.2 mV in darkness.

[3]

- (c) A strain gauge is securely fixed to a loaded cylinder wall under strain test and connected to a circuit as shown in Fig. 2.2.

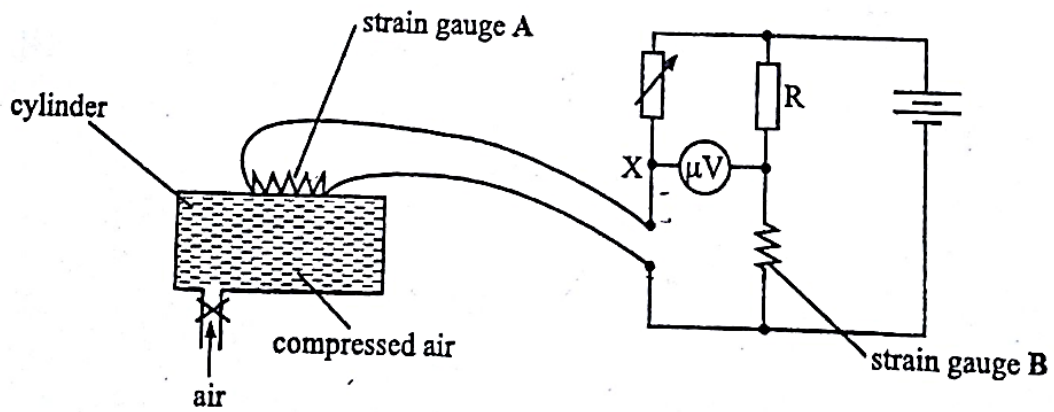


Fig. 2.2

- (i) Describe and explain the changes in potential at X as the amount of compressed air is increased.
- (ii) State the advantage of using two strain gauges in this arrangement.
- (iii) Suggest another practical use of a similar circuit to that in Fig. 2.2.

9188/5 N2014

[5]