

Q1:JUN 2008 P2

8 Fig. 8.1 shows a logic circuit.

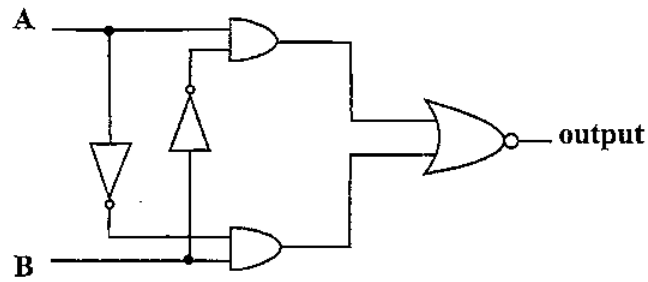


Fig. 8.1


(i) Draw a truth table for the circuit. [4]

(ii) Identify a single gate which is equivalent to the circuit. [1]

Q2:NOV 2013 P2

7 (a) Define a logic gate. [1]

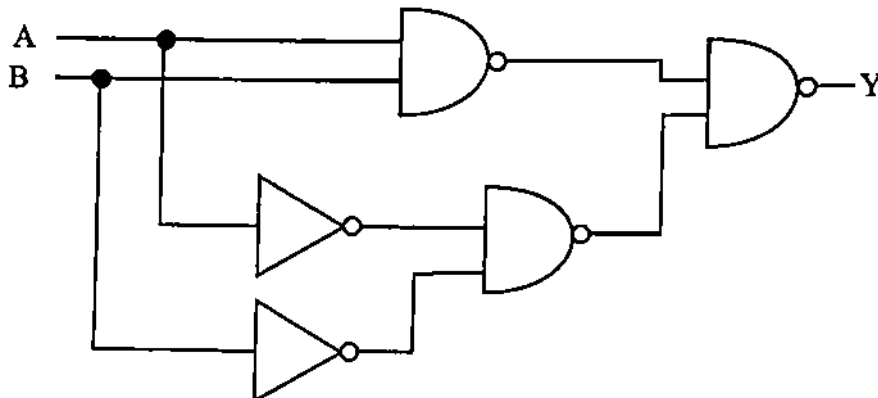(b) Fig. 7.1 shows a combination of logic gates.



Q3: NOV 2015 P2

- 7 (a) Define a logic gate.

[1]

- (b) Fig.7.1 shows a combination of logic gates.

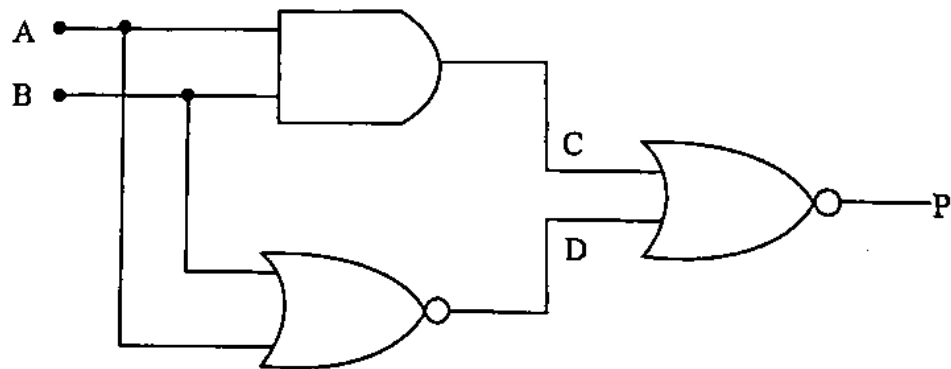


Fig.7.1

- (i) Construct a truth table for the combination.

- (ii) State the logical function for the combination.

[4]

Q4:NOV 2018 P2

7 Fig. 7.1 shows a combination of logic gates.

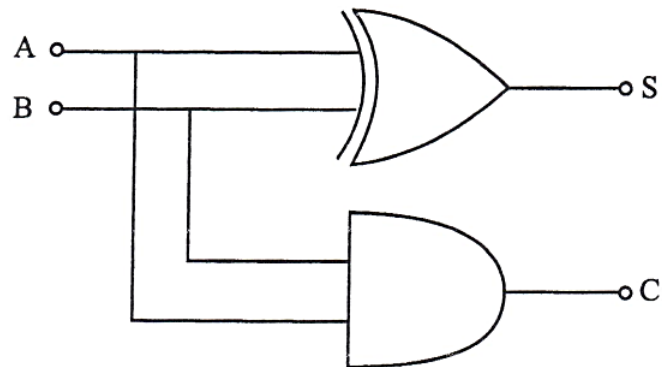


Fig. 7.1

(a) Name the logic gates used.

[1]

(b) Complete the truth table for the circuit in Fig.7.1.

A	B	C	S
0	0		
0	1		
1	0		
1	1		

[2]

Q5:JUN 2007 P3

- 5 (a) (i) Draw the symbol of a 2-input **OR** gate. [2]
 (ii) Write down its truth table.
 (b) (i) Draw a truth table for the circuit shown in Fig. 5.1.

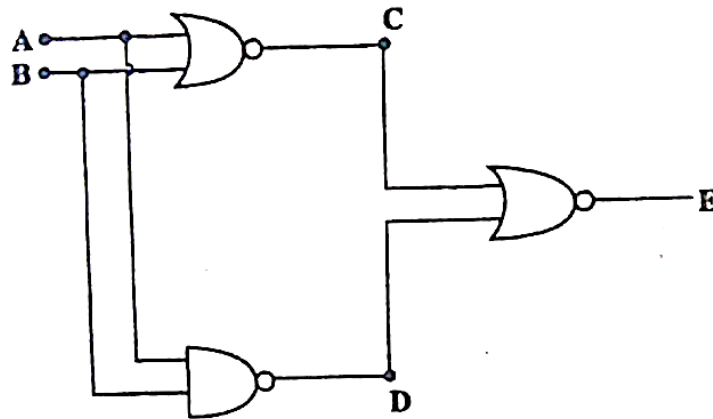


Fig. 5.1

- (ii) State the name given to a gate which behaves as the circuit in b(i). [4]
 (c) Table 5.1 shows the characteristics of an LDR.

Table 5.1

Resistance/ $k\Omega$	0.1	1.0	10	100	1 000
Intensity/ Wm^{-2}	100	10	1.0	0.1	0.01

The LDR is incorporated into the circuit of Fig. 5.2.

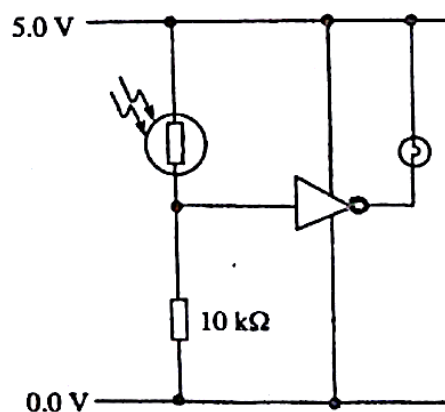


Fig. 5.2

- (i) Explain how the circuit works.
 (ii) Deduce from Table 5.1 the range of the light intensity in which the bulb lights.

- (iii) Suppose the bulb is placed close to the LDR and the system is initially in the dark. Explain what happens when a torch is briefly shone on the LDR.
- (iv) Explain one application of the circuit in Fig. 5.2. [9]
- (d) The circuit of Fig. 5.2 was modified as in Fig. 5.3.

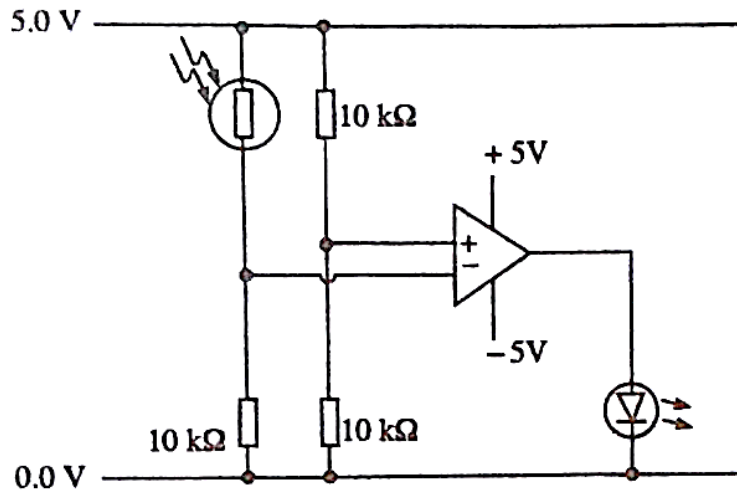


Fig. 5.3

- (i) Identify the circuit.
- (ii) Calculate the potential at A when the light intensity on the LDR is 10 Wm^{-2} .
- (iii) Deduce the conditions under which the LED will light. [5]

Q6:NOV 2006 P3

- 5 (c) Fig. 5.1 shows a combination of logic gates.

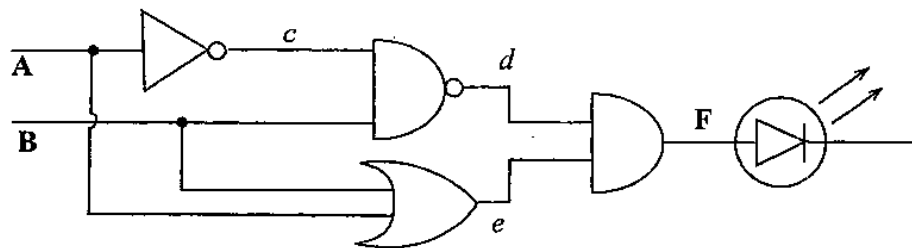


Fig. 5.1

Show that the output of the L.E.D is independent of the state of B. [4]

- (d) Fig. 5.2 shows a two way switch.

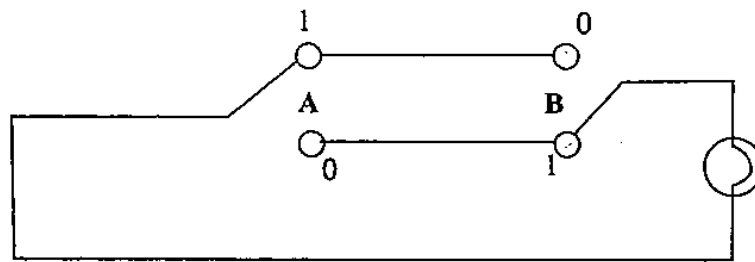


Fig. 5.2

- (i) Draw a truth table to show how this switch operates.
 - (ii) Give **one** gate that is represented by this circuit. [3]
- (e)
- (i) Name **one** electronic device and **one** analogue device that perform the same functions.
 - (ii) Give **two** advantages of the electronic device. [4]

Q7:NOV 2009 P5

- 5 (c) Fig. 5.2 shows three logic gates connected together.

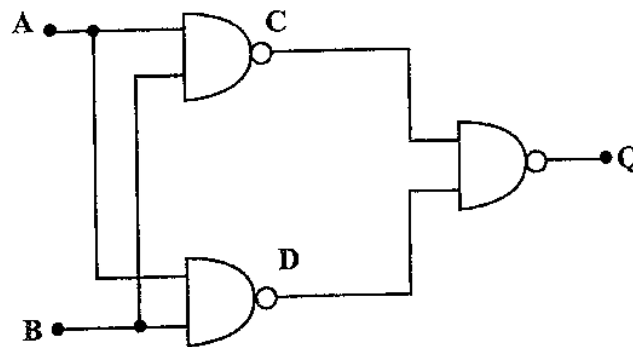


Fig. 5.2

- (i) Give the name of the logic gates used.
- (ii) Draw the truth-table for the circuit shown.
- (iii) Write down the name of a single logic gate that performs the same function as the circuit in Fig. 5.2. [5]

Q8:NOV 2012 P5

- 4 (a) (i) Write down the truth table for a two input Exclusive OR gate [3]
 (ii) Construct a combination of NAND gates to form an Exclusive OR gate [3]
 (b) Draw the truth table for the logic circuit shown in Fig.4.1. [6]

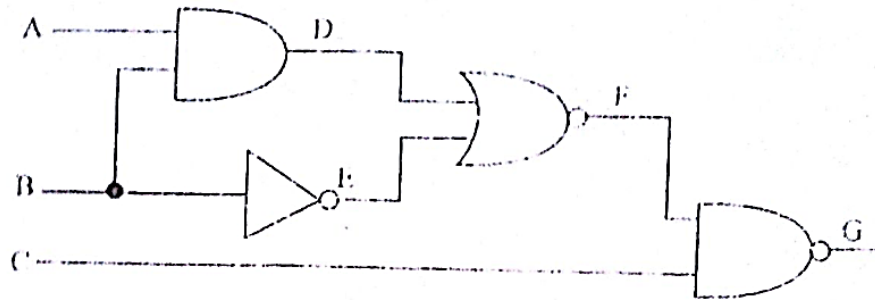


Fig. 4.1

- (c) Receiving information of events in the world such as sporting news and natural disasters is almost instantaneous.

State three aspects of modern communication which have made this possible.

[3]

Q9:JUN 2010 P5

- 5 (a) Fig. 5.1 shows an alarm circuit to wake up school children in the morning.

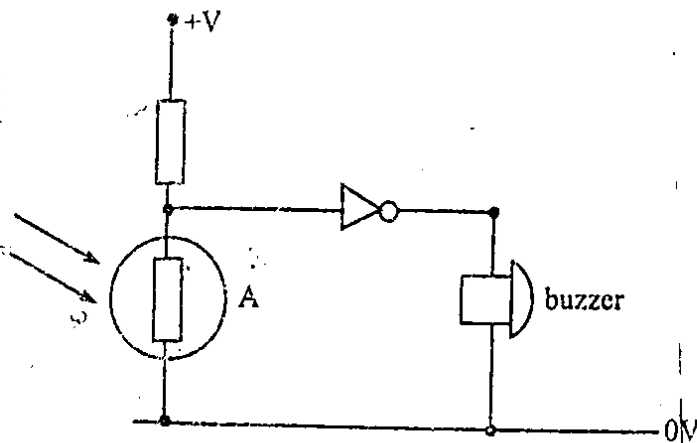


Fig. 5.1

- (i) State the name of component A.
 (ii) Describe and explain how the circuit operates.
 (iii) Draw a truth table for the circuit.

[7]

5.2 DIGITAL ELECTRONICS P2, P3&P5 QUESTIONS

Compiled by : *R. Muga* +268 776 162 075

- (b) Briefly outline **three** positive and **two** negative impacts of modern electronic technology on society.

[5]

Q10:JUN 2011 P5

- 5 (a) Describe the use of an Operational Amplifier as a summing amplifier in the inverting mode. [3]
- (b) The circuit shown in Fig. 5.1 is a simple combination locking system which will allow access to a bank safe if the correct combination is set to A, B, C and D. If there is any wrong combination the alarm will sound.

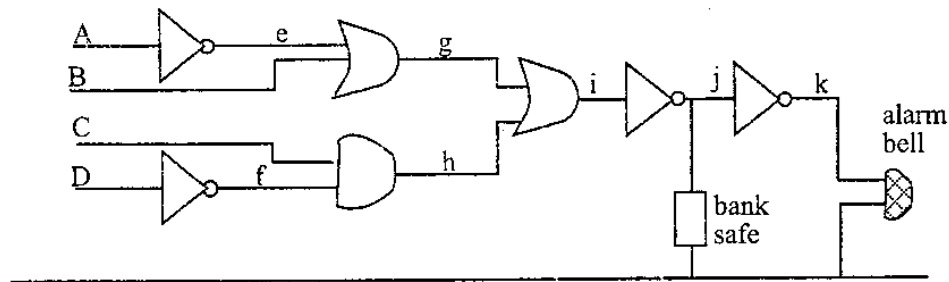


Fig. 5.1

- (i) Work out the correct codes to open the bank safe.
- (ii) Give **one** advantage of this method. [5]
- (c) Describe the three parts of a radio system in terms of the *input, electronic circuit* and the *output device*. [3]
- (d) State **one** negative impact of electronics in society. [1]

Q11:JUN 2018 P5

- 5 (a) Fig.5.1 represents a vehicle alarm system.

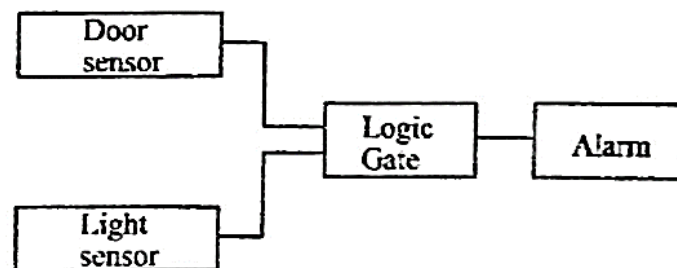


Fig.5.1

The system should be such that the alarm sounds when either the door is open or the light is on or both.

- (a) Identify a suitable
1. light sensor,
 2. logic gate,
 3. output transducer.

[3]

Q12:JUN 2019 P3

- 3 (d) Fig. 3.4 shows a combination of logic gates.

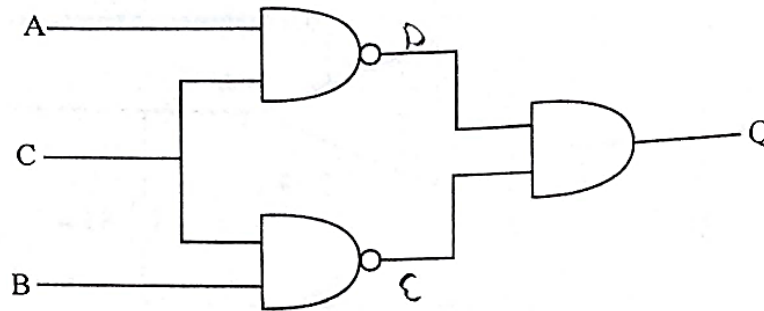


Fig. 3.4

Input C is maintained at logic level 1.

- (i) Construct the truth table for the combination.
- * (ii) Hence deduce the single logic gate that is equivalent to the combination.

[4]